

**Department of Computer Science and Engineering. NITK, Surathkal**  
**CS203 – Design of Digital Systems Lab**

**Assignment 2**

Simulate the listed experiments on LogiSim (<https://sourceforge.net/projects/circuit/>).

Instructions:

1. Assignment is to be completed in teams of 2. One submission per team.
2. Submission: Create a directory with the registration numbers of your team. Eg. 18CO201-202. Inside,
  - a. place a README with your identification info (name, reg. No. etc., ...).
  - b. Create one directory per question. Put your code, screenshots, etc. inside the directory.
3. Pack the parent directory and send to [cs201.nitk@gmail.com](mailto:cs201.nitk@gmail.com). Deadline: September 11, 9AM.

**Experiments to Simulate on LogiSim (Module III)**

1. Verify the truth tables for the following gates: AND, OR, NOT, NAND, NOR, XOR, XNOR.
2. Implement all the gates in Q1 using universal gates (NANDs and NORs)
3. Find  $r$ 's and  $(r-1)$ 's complement of a given number using Universal gates only.
4. Implement
  - a. Gray code to Binary code and vice versa.
  - b. Excess-3 to BCD code and vice versa.
  - c. Output binary number equal to the square of the input number.
  - d. 9's complement of decimal equivalent of BCD.
5. Implement (i) Half Adder (ii) Half Subtractor (iii) Full Adder (iv) Full Subtractor
6. Implement
  - a. 4-bit adder using decoder
  - b. 4-bit adder using multiplexer
  - c. 4-bit subtractor using decoder
  - d. 4-bit subtractor using multiplexer